

# Fundamentals of Digital Logic Design

ECE/CS 3700

Spring 2013, Homework # 4

Due Date: Mon, April 1, 5pm sharp, due in the HW locker.

- 1) (15 points) **Propagate-generate-delete signals in adders.** In class, we studied the carry look-ahead adder as a means to speed-up carry propagation delay of the ripple carry adder. Look-ahead adders make use of the generate ( $G_i$ ) and propagate ( $P_i$ ) signals to *precompute* whether or not stage  $i$  would output a carry. Similar to using the propagate ( $P_i$ ) and generate ( $G_i$ ) signals, a look-ahead adder can be designed by using a propagate ( $P_i$ ), generate ( $G_i$ ) and delete ( $D_i$ ) signal. Consider the Truth table of the full adder shown in Table I:

TABLE I  
TRUTH TABLE OF A FULL ADDER

$a$	$b$	$c_i$	$S$	$c_{i+1}$	Carry Status
0	0	0	0	0	Delete
0	0	1	1	0	Delete
0	1	0	1	0	Propagate
0	1	1	0	1	Propagate
1	0	0	1	0	Propagate
1	0	1	0	1	Propagate
1	1	0	0	1	Generate
1	1	1	1	1	Generate

The first two minterms  $m_0, m_1$  correspond to the condition where the carry-out signal gets suppressed (deleted) at  $c_{i+1}$ , independent of the value at  $c_i$ . Prove that:

- The Delete signal  $D_i = a' \cdot b'$ .
- $Sum = P_i \cdot \overline{C_i} + D_i \cdot C_i + G_i \cdot C_i$
- $C_{i+1} = G_i + \overline{D_i} \cdot C_i$ .

- 2) (10 points) Given that  $A, B, C_i$  are the inputs to a full adder,  $S$  and  $C_o$  are sum and carry-out, respectively, prove that:

- $S = ABC_i + \overline{C_o}(A + B + C_i)$ .

- 3) (25 points) **Multiplier design.** You are asked to design an array multiplier that multiplies a 4-bit number  $A = (a_3, a_2, a_1, a_0)$  by a 3-bit number  $B = (b_2, b_1, b_0)$ . Consider that pre-designed 4-bit adders are available to you. (Recall that a 4-bit adder adds two four-bit numbers). Design the multiplier using only **two 4-bit adders** and a minimum number of two-input AND/OR/NOT/XOR/XNOR gates. Show a block diagram or a schematic of your design depicting input and output bits clearly. (Solve this problem properly, and you've understood the concept of array multipliers!).

- 4) (15 points) **Two's complement numbers.** Suppose that you are given two **3-bit unsigned** numbers  $A[2 : 0]$ ,  $B[2 : 0]$  that have to be added together ( $C = A + B$ ). Suppose, further, that you are given a pre-designed *4-bit adder* that you have to use for this purpose. A 4-bit adder takes inputs  $X[3 : 0]$ ,  $Y[3 : 0]$  and adds them. In order to do the addition correctly, we can take vectors  $A, B$  and concatenate a leading 0 to make them 4-bit vectors and then map the inputs; i.e. in Verilog terms:  $X[3 : 0] = \{1'b0, A[2 : 0]\}$ ; and similarly  $Y[3 : 0] = \{1'b0, B[2 : 0]\}$ . This way,  $n$ -bit unsigned integers can be scaled to larger bits.

However, this technique may not work for 2's complement scheme. So, now you have to answer the following: You are given two 3-bit vectors  $A[2 : 0]$ ,  $B[2 : 0]$  that are already given in **3-bit two's complement form**. You are asked to subtract  $A - B$ . Suppose that you are already given a *4-bit subtractor* (say, the design of Fig. 5.13, pp. 248 in the textbook) that takes  $X[3 : 0]$ ,  $Y[3 : 0]$  and computes  $C = X - Y$ , where  $C$  is a 4-bit two's complement number. You have to use this 4-bit subtractor to subtract the given 3-bit numbers  $A, B$ . How will you scale (or modify) the inputs correspondingly? Show your design/schematic (or a Verilog code, if you wish), and demonstrate the correct functioning of your circuit using an example.

- 5) (10 points) **Decoders.** Solve problem 6.1, pp. 375, from the textbook.
- 6) (10 points) **Shannon's Expansion and MUXes.** Solve problem 6.5, pp. 375, from the textbook.
- 7) (15 points) **A practical example of Code-Converters.** Braille is a system of raised dots that can be read by a blind person. You are asked to design an *encoder* circuit that converts Binary Coded Decimal (BCD) numbers to Braille. The Braille patterns for the BCD numbers are shown below in Fig. 1.

 


Fig. 1. Braille representation of digits 0 to 9.

Derive a minimum sum-of-product form representation for each of the four Braille dot outputs  $X, Y, W, Z$  in terms of a 4-bit BCD number. Denote the 4-bit BCD number as  $ABCD$  where  $A$  is the most significant bit, and  $D$  the least significant bit.